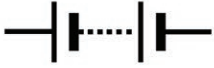

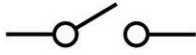







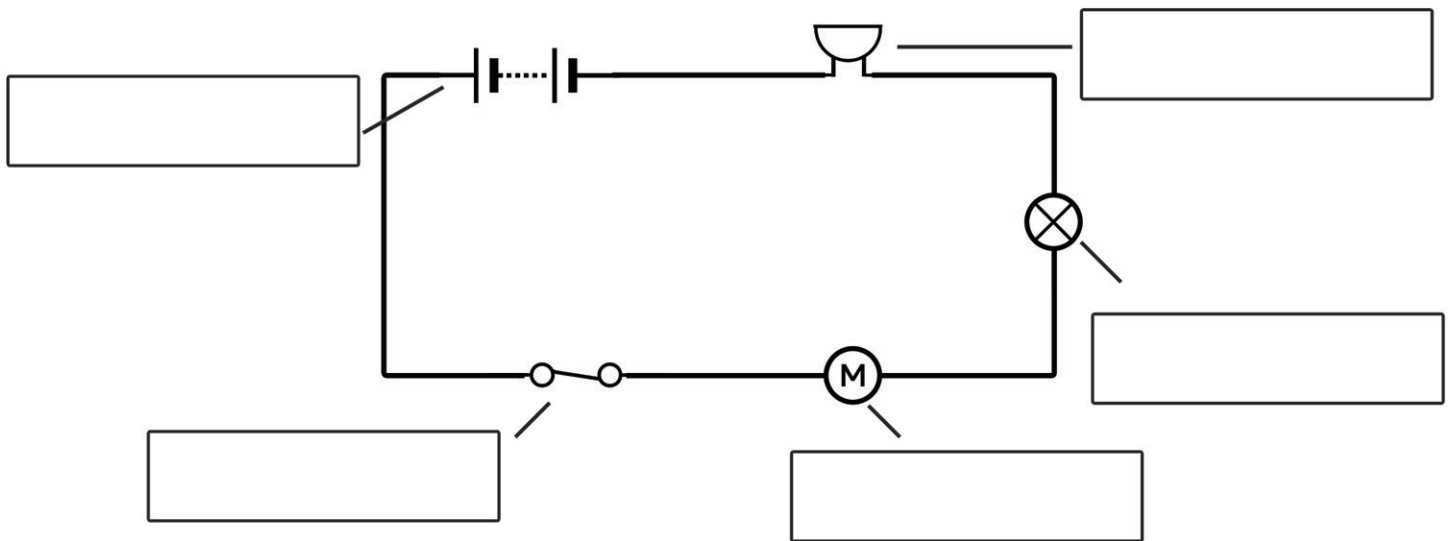


# Electric Circuits

Electricity flows in a circuit from the positive pole of a battery to its negative pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 lamp	 lamp	 motor	 wire

Label the circuit below.



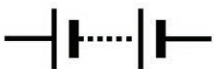

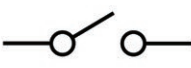




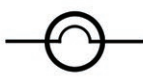
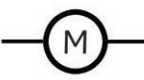

Complete the sentences.

The electric current leaves the \_\_\_\_\_ and passes through the \_\_\_\_\_.

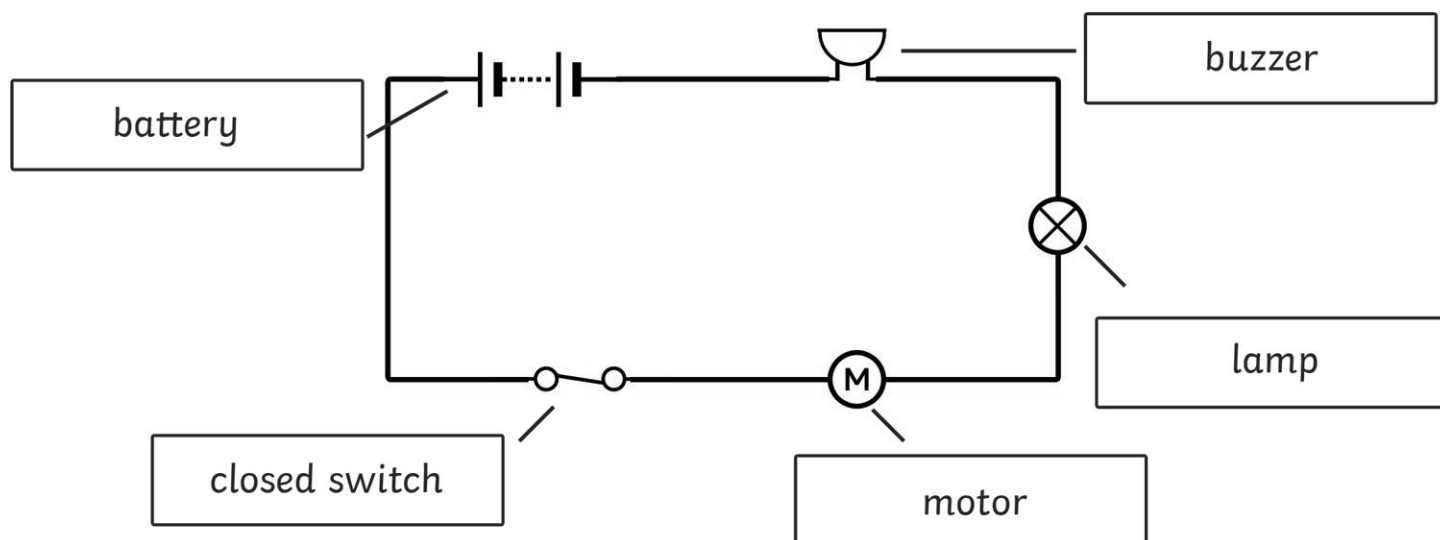
It then travels through the \_\_\_\_\_, next through the \_\_\_\_\_ and finally through the \_\_\_\_\_ before returning to the battery.

# Electric Circuits - Answers

Electricity flows in a circuit from the positive pole of a battery to its negative pole. The flow of electricity creates an electric current. There is a symbol to represent each component in an electrical circuit.

 battery	 closed switch	 open switch	 cell	 voltmeter
 buzzer	 lamp	 lamp	 motor	 wire

Label the circuit below.



Complete the sentences.

The electric current leaves the battery and passes through the closed switch.

It then travels through the motor, next through the lamp and finally through the buzzer before returning to the battery.