

Conductors & Insulators

Design a circuit that you could use to investigate if an object is a conductor or an insulator. To be able to do this, you will need to make sure that there is power in your circuit and that there is a way to tell if electricity is passing around the circuit.

My circuit