


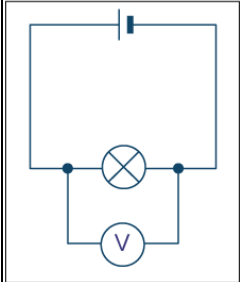


Electricity True or False?

	STATEMENT	YES	NO	MAKE IT RIGHT
1	Current is measured in units called volts.			
2	 <p>This is the symbol used to represent a battery.</p>			
3	If one of the bulbs in a series circuit breaks, none of the bulbs will light up.			
4	All of the bulbs in a parallel circuit will be the same brightness, provided they all have the same resistance.			
5	To measure the voltage across a power source you need to arrange the voltmeter in series.			
6	 <p>This is the symbol used to represent a lamp in a circuit.</p>			
7	The resistance of a bulb is equal to the current flowing through it divided by the voltage.			
8	 <p>The short line represents the positive terminal.</p>			
9	 <p>If the resistance of the bulb is 2 ohms, and the current is 5amps the voltage will be 2 volts.</p>			