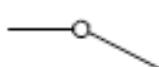
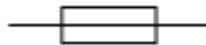
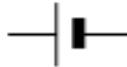
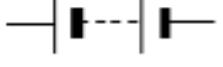
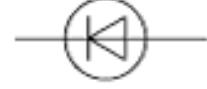
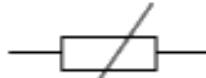
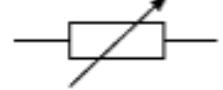
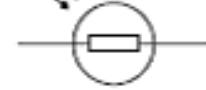


Symbols used in electrical circuits

	switch (open)		lamp
	switch (closed)		fuse
	cell		voltmeter
	battery		ammeter
	diode		
	resistor		thermistor
	variable resistor		LDR